

Incubator Shield

This circuit connects an Arduino to the components of a desktop incubator that can sustain a temperature of 100F safely for several days. Intended for tempeh...


12V Power

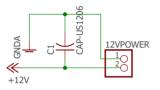


Arduino Connections

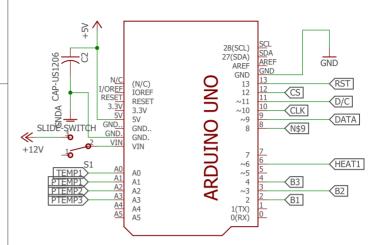

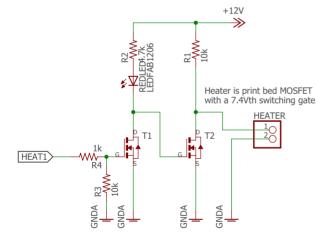
Heated Bed Logic Shifter (noninverting/ norm-off)



OLED Display (sSPI)

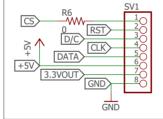

Thermistor

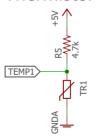

Buttons

